

Design of 8X3 Priority Encoder

Group Number: 21

Guided By:
Dr. Anuj Grover
Ali & Aditya

Group Members:
Amisha (MT25160)
Dushyant (MT25115)
Aditya (2023044)
Ronak (2023447)



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY **DELHI**


Schematic + Sizing





$$A = D7 + D6 + D5 + D4$$

$$B = D7 + D6 + D5' D4' (D3 + D2)$$

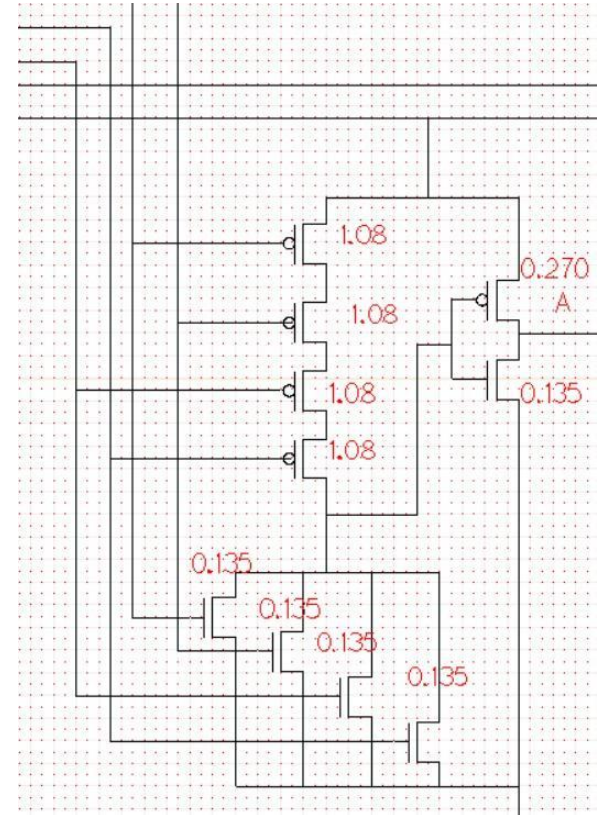
$$C = D7 + D6' (D5 + D4' D3 + D4' D3' D2' D1)$$



Schematic + Sizing

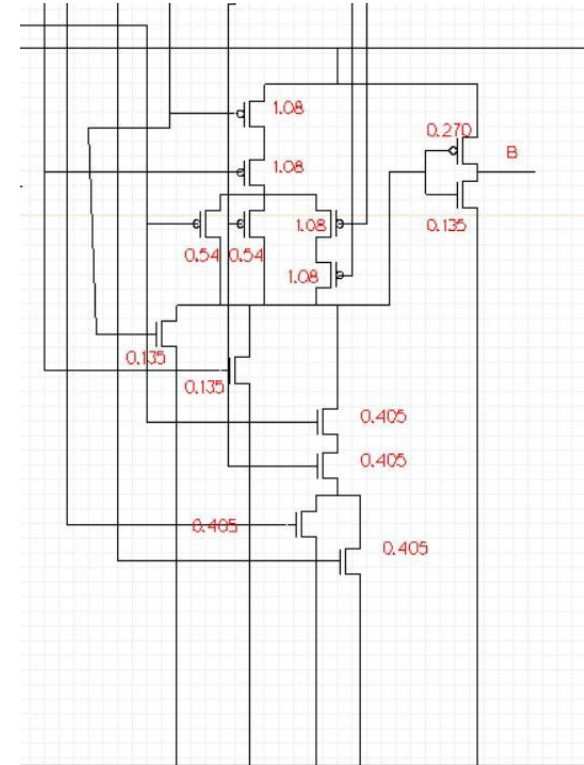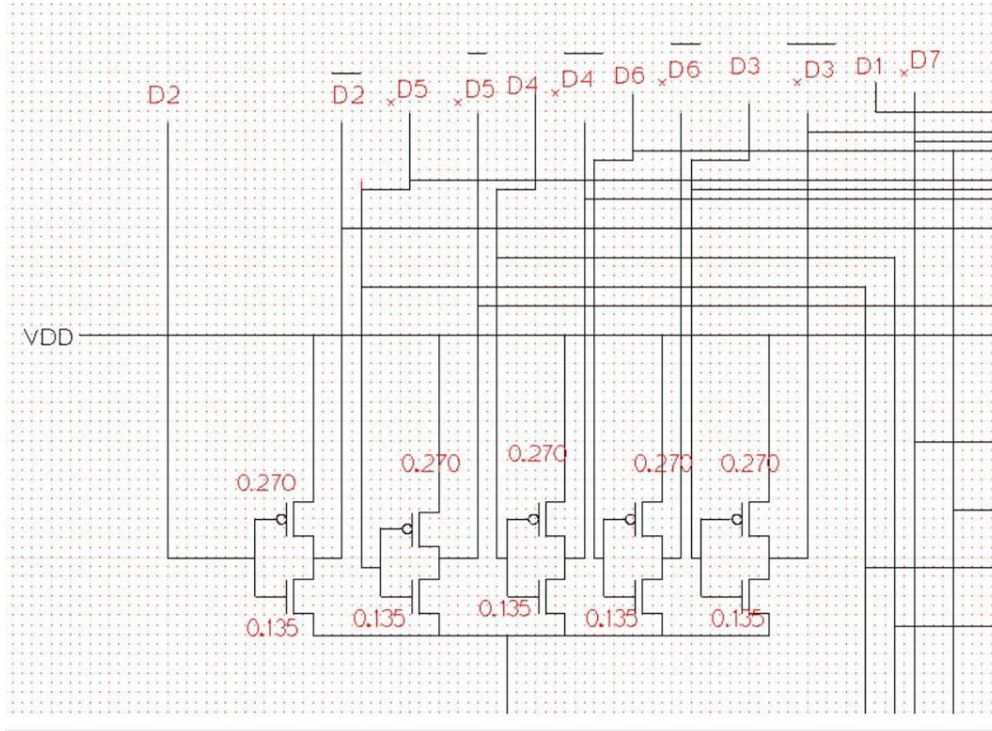

Schematic + Sizing

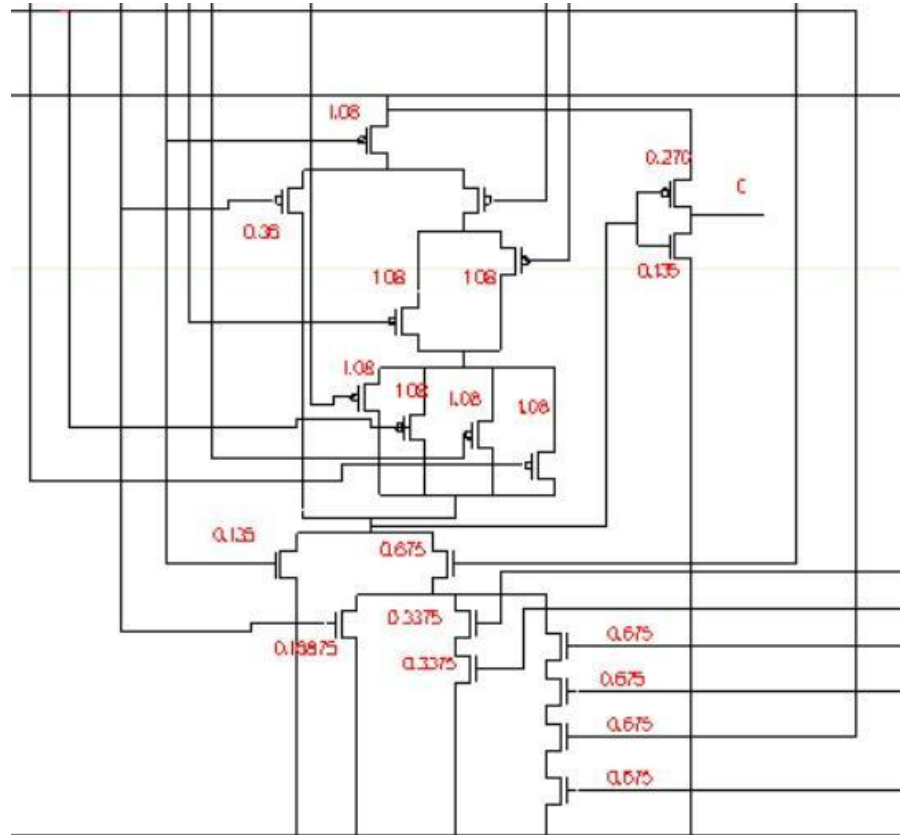

Stimuli For Verification & Verification Plan



```
.include /modelfile_65nm/minNminP.cir
*.include /modelfile_65nm/typNtypP.cir

.include PROJECT2.src.net

*from netlist
X1 A B C D1 D2 D3 D4 D5 D6 D7 Gnd Vdd PROJECT

.param SUPPLY = 1.08
.Param tend = 150n

.TEMP = 125

c1 A Gnd 10f    *Load capacitance
c2 B Gnd 10f
c3 C Gnd 10f

vd Vdd 0 SUPPLY
vg Gnd 0 0

*v0 D0 Gnd PULSE(0 SUPPLY 1n 10p 10p 5n 20n)
v1 D1 Gnd PULSE(0 SUPPLY 1n 10p 10p 5n 20n)
v2 D2 Gnd PULSE(0 SUPPLY 3n 10p 10p 5n 20n)
v3 D3 Gnd PULSE(0 SUPPLY 5n 10p 10p 5n 20n)
v4 D4 Gnd PULSE(0 SUPPLY 7n 10p 10p 5n 20n)
v5 D5 Gnd PULSE(0 SUPPLY 9n 10p 10p 5n 20n)
v6 D6 Gnd PULSE(0 SUPPLY 11n 10p 10p 5n 20n)
v7 D7 Gnd PULSE(0 SUPPLY 13n 10p 10p 5n 20n)
```

```
aditya23044@edatools-server2
File Edit View Search Terminal Help

TPLH_A = 1.6594E-10
TPLH_B = 2.0486E-10
TPLH_C = 2.5205E-10
TPHL_A = 2.2327E-10
TPHL_B = 2.7980E-10
TPHL_C = 3.0033E-10

SIMULATION INFORMATION
memory size allocated in Mbytes 260.2
Latency: 0.000000%
average number of newton iterations: 3.008103
nb of components: 66
nb of nodes: 90
nb of MOS or BIP calls: 112188
Number of steps computed: 2098

***>CPU TIME 0s 420ms <***

***>MESSAGE SUMMARY: 4 warnings

***>GLOBAL CPU TIME 0s 630ms <***

***>GLOBAL ELAPSED TIME 3s <***
```

Stimuli For Verification & Verification Plan



```

*.include /modelfile_65nm/minNminP.cir
.include /modelfile_65nm/typNtypP.cir

.include PROJECT2.src.net

*from netlist
X1 A B C D1 D2 D3 D4 D5 D6 D7 Gnd Vdd PROJECT

.param SUPPLY = 1.08
.Param tend = 150n

.TEMP = 125

c1 A Gnd 10f *Load capacitance
c2 B Gnd 10f
c3 C Gnd 10f

vd Vdd 0 SUPPLY
vg Gnd 0 0

*v0 D0 Gnd PULSE(0 SUPPLY 1n 10p 10p 5n 20n)
v1 D1 Gnd PULSE(0 SUPPLY 1n 10p 10p 5n 20n)
v2 D2 Gnd PULSE(0 SUPPLY 3n 10p 10p 5n 20n)
v3 D3 Gnd PULSE(0 SUPPLY 5n 10p 10p 5n 20n)
v4 D4 Gnd PULSE(0 SUPPLY 7n 10p 10p 5n 20n)
v5 D5 Gnd PULSE(0 SUPPLY 9n 10p 10p 5n 20n)
v6 D6 Gnd PULSE(0 SUPPLY 11n 10p 10p 5n 20n)
v7 D7 Gnd PULSE(0 SUPPLY 13n 10p 10p 5n 20n)

```

File	Edit	View	Search	Terminal	Help
------	------	------	--------	----------	------

```

TPLH_A = 1.3530E-10
TPLH_B = 1.5730E-10
TPLH_C = 1.8986E-10
TPHL_A = 1.7883E-10
TPHL_B = 2.1911E-10
TPHL_C = 2.3079E-10

SIMULATION INFORMATION
memory size allocated in Mbytes 260.2
Latency: 0.000000%
average number of newton iterations: 3.024964
nb of components: 66
nb of nodes: 90
nb of MOS or BIP calls: 111223
Number of steps computed: 2083

***>CPU TIME 0s 460ms <***


***>MESSAGE SUMMARY: 4 warnings

***>GLOBAL CPU TIME 0s 670ms <***



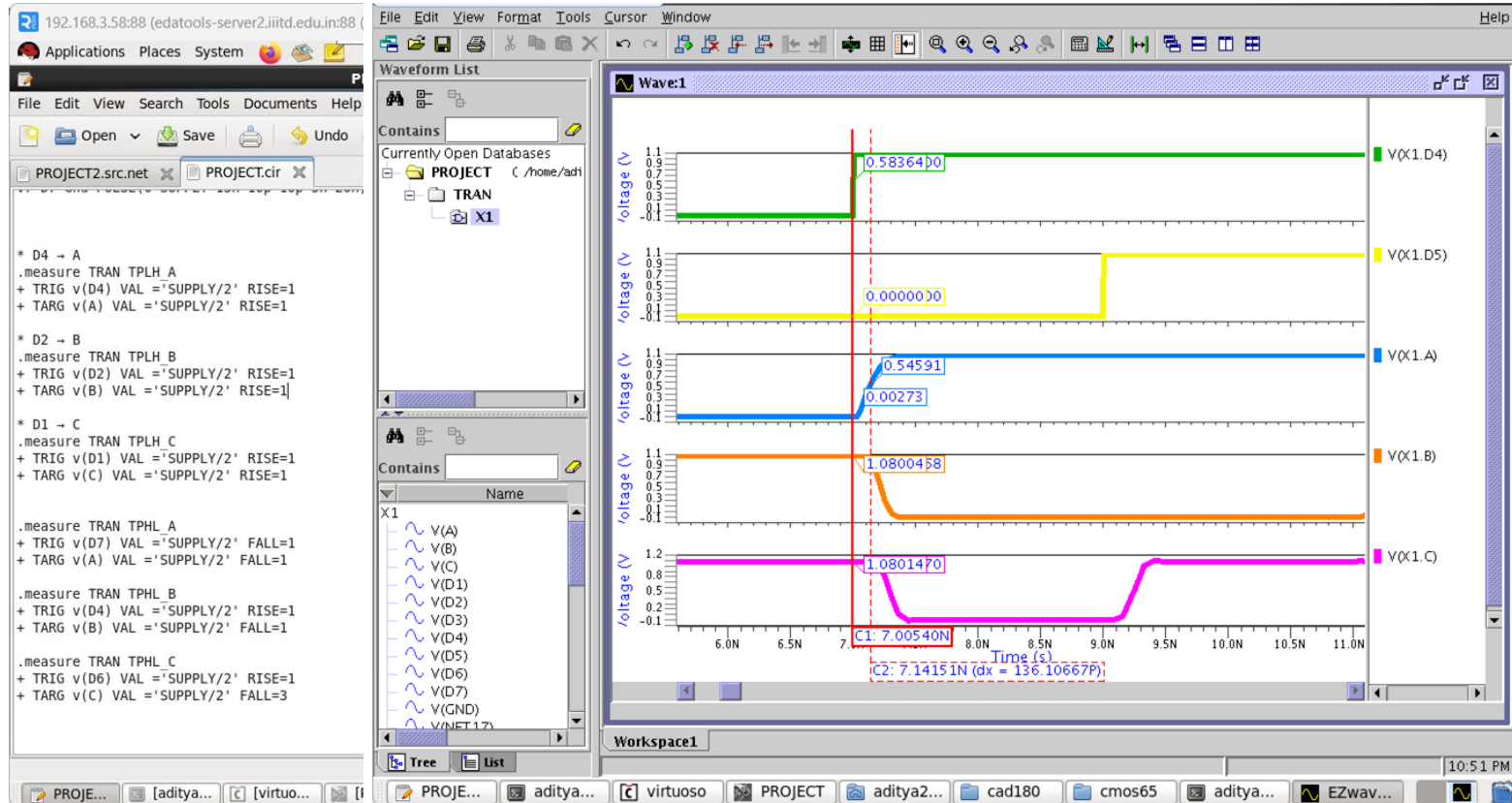
***>GLOBAL ELAPSED TIME 3s <***

```


Stimuli For Verification & Verification Plan



Stick diagram

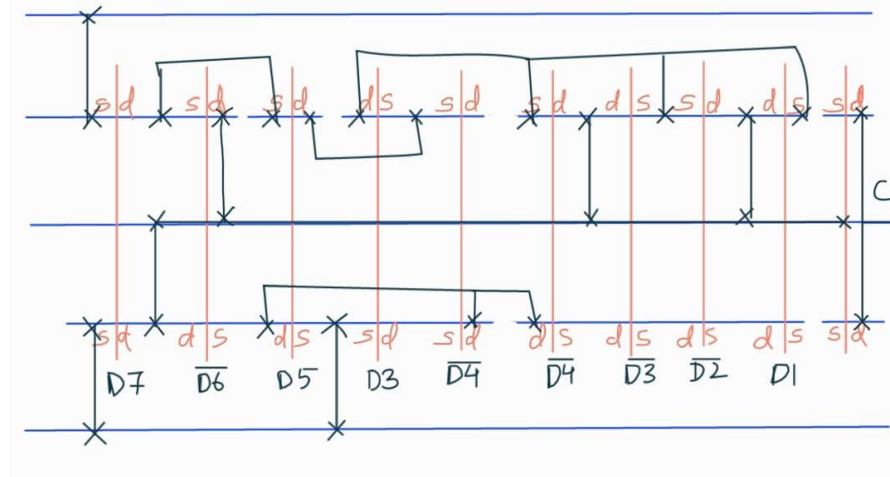  

Future Work + Work Distribution



Amisha	Virtuoso Schematic, debugging & stick diagram
Dushyant	Functional verification & delay calculation
Aditya	Schematic & functional verification
Ronak	XCircuit schematic & sizing

Future Work Plans:

1. Power calculation
2. Stick diagram optimization & Layout
3. Post layout simulations